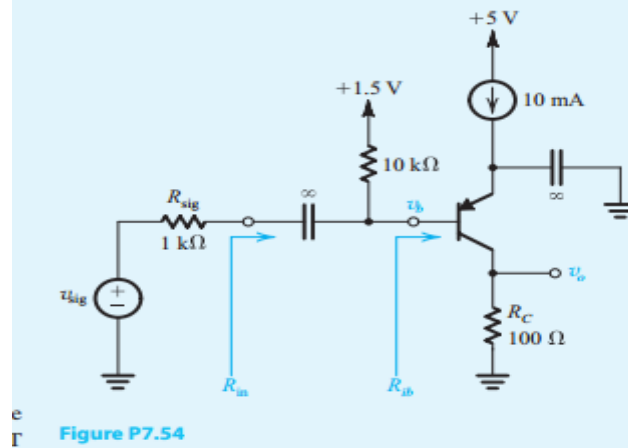


الاسم : احمد علاء الدين ابو الفتوح


Sec: 1 B.n:5

Problem (7.54)

7.54 In the circuit shown in Fig. P7.54, the transistor has a β of 200. What is the dc voltage at the collector? Replacing the BJT with one of the hybrid- π models (neglecting r_o), draw the equivalent circuit of the amplifier. Find the input resistances R_{ib} and R_{in} and the overall voltage gain (v_o/v_{sig}). For an output signal of ± 0.4 V, what values of v_{sig} and v_b are required?



Simulation

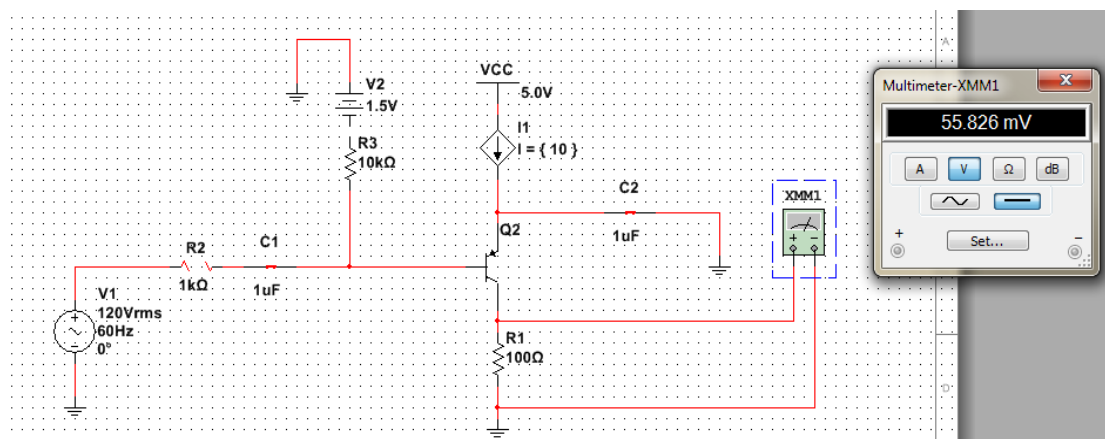

Solution

DC analysis

Problem 7.54

1.5V

10k Ω

Base

5V

Emmitter

10mA

I_B

V_{BE}

I_E

$\beta = 200$

$r_o = \infty$

Base

I_C

Collector

100 Ω

Collector

V_o

$I_E = 10\text{mA}$

$I_E = \beta I_B$

$I_E = (B+1) I_B$

$10 = (200+1) I_B$

$\therefore I_B = 0.0497\text{mA}$

$\therefore I_C = 200(0.0497)$

$= 9.95\text{mA}$


$g_m = \frac{I_C}{V_T}$

$\therefore g_m = \frac{9.95}{0.025}$


$= 398\text{mA/V}$

$K_T = \frac{200}{398} = 0.502\text{k}\Omega$

AC analysis

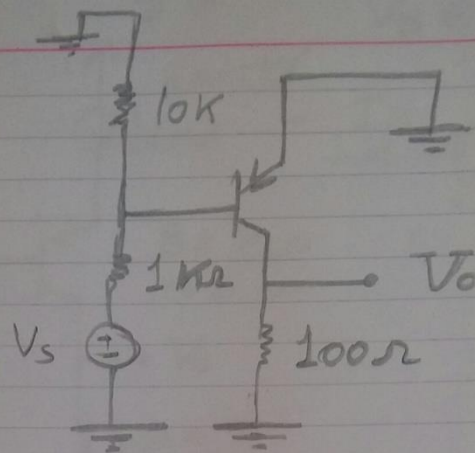

Hybrid- π model

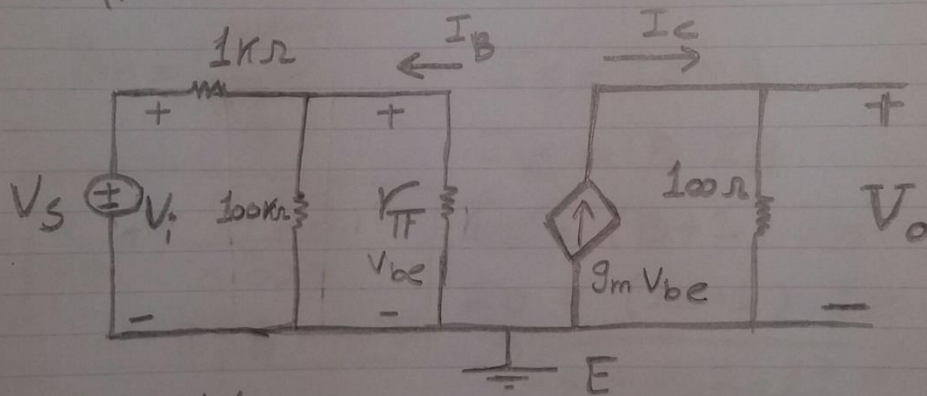

$$A_v = \frac{V_o}{V_i}$$

$$V_{be} = \frac{V_i * \left(\frac{100 * 0.502}{100 + 0.502} \right)}{1 + \left(\frac{100 * 0.502}{100 + 0.502} \right)}$$

$$\therefore \boxed{V_{be} = 0.333 V_i}$$

$$\therefore V_o = 13.25 V_i$$

$$V_o = g_m V_{be} * 0.1$$

$$\therefore \boxed{A_v = \frac{V_o}{V_i} = 13.25}$$

$$= (398)(0.333 V_i)(0.1) = 13.25 V_i$$

Excel

L	K	J	I	H	G	F	E	D	C	B	A
				constants				vt	vee(mv)	vdd(mv)	
									0.025	1.5	5
Av	vbe	rpi(kohm)	gm(ma/v)	IC(ma)	IB(ma)		R2(kohm)	rsg(kohm)	R1(KOHM)	IE(ma)	B
13.26678	0.333328	0.5025	398.01	9.950249	0.049751		0.1	1	100	10	200
7.967969	0.201191	0.2525	396.0396	9.90099	0.09901		0.1	1	100	10	100
9.925312	0.498747	1.005	199.005	4.975124	0.024876		0.1	2	100	5	200
66.11352	0.33222	0.5025	398.01	9.950249	0.049751		0.5	1	50	10	200
Out put parameters						Input varied parameters					